Esercizio 1

Tabella di verità:

Input(decimale)	Α	В	С	LED1	LED2	LED3	LED4	LED5
0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0	0
2	0	1	0	0	1	0	1	0
3	0	1	1	0	1	1	1	0
4	1	0	0	1	1	0	1	1
5	1	0	1	1	1	1	1	1
6	1	1	0	х	х	х	х	х
7	1	1	1	х	х	х	х	х

LED1:

C\AB	00	01	11	10
0	0	0	0	1
1	0	0	0	1

1 = AB

LED2:

C\AB	00	01	11	10
0	0	1	Χ	1
1	0	1	Х	1

 $2 = A + \overline{A} B$

LED3:

C∖AB	00	01	11	10
0	0	0	Χ	0
1	1	1	Х	1

3 = C

LED4:

C\AB	00	01	11	10
0	0	1	Χ	1
1	0	1	Χ	1

$4 = \overline{A} B + A LED5$:

C\AB	00	01	11	10
0	0	0	Χ	1
1	0	0	Х	1

5 = AB